

Name of the Experiment:

DESIGN AND IMPLEMENTATION OF MOD-10 COUNTER.

Objectives:

1) used in digital electronics for counting purpose.

Theory:

Counter: A counter is a device which stores (and sometimes displays) the number of times a particular event or process has occurred, often in relationship to a clock signal. Counters are used in digital electronics for counting purpose, they can ^{Count} specific event happening in the circuit. Not only counting, a counter can follow the certain sequence based on our design like any random sequence 0, 1, 2, 3, 4, They can also be designed with the help of flip-flops.

Counters are sequential circuit that count the number of pulses can be either in binary code or BCD form. The main properties of a counter are timing, sequencing, and counting.

A decade counter counts ten different states and then reset to its initial states. A simple decade counter will count from 0 to 9, ~~but~~

Apparatus:

- i) 2 J K Flip-Flops (IC 7476)
- ii) NAND gate (IC 7400)
- iii) Connecting wires
- iv) Breadboard
- v) Trainer board

Pin Configuration of IC 7476:

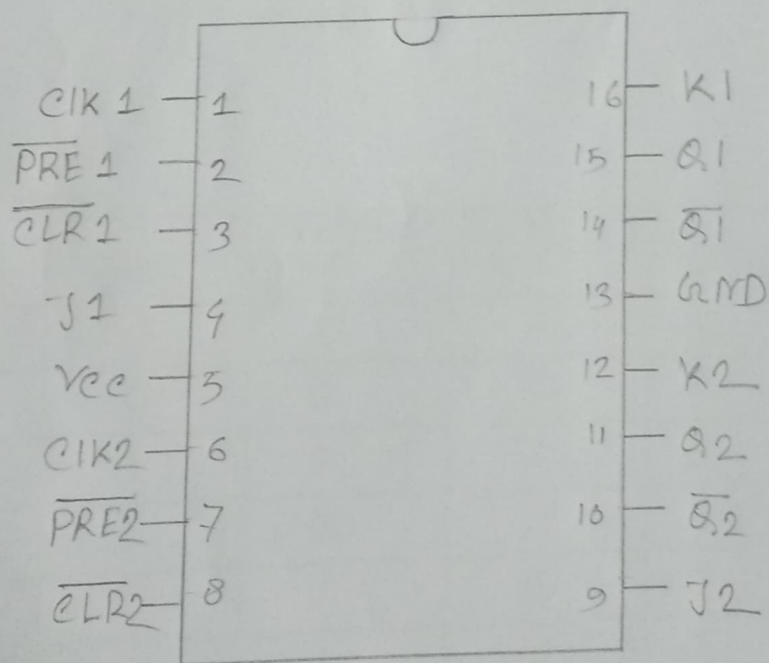


Figure: IC 7476 Pin diagram

Circuit Diagram:

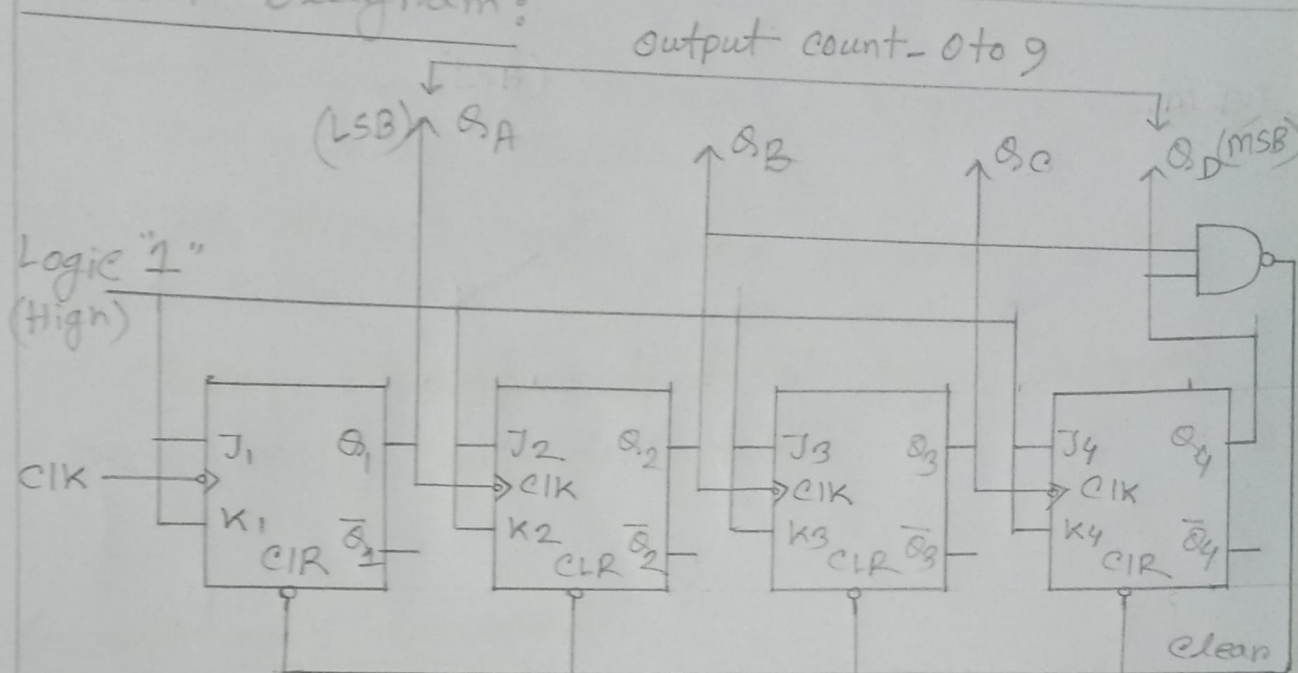


Fig: Mod-10 Counter

Truth Table:

Clock Count	Output Pattern bit				Decimal value
	Q _D	Q _C	Q _B	Q _A	
1	0	0	0	0	0
2	0	0	0	1	1
3	0	0	1	0	2
4	0	0	1	1	3
5	0	1	0	0	4
6	0	1	0	1	5
7	0	1	1	0	6
8	0	1	1	1	7
9	1	0	0	0	8
10	1	0	0	1	9
11	Counter Resets its output back to zero				

working procedure:

- i) implemented the circuit diagram according to the circuit diagram.
- ii) Logic inputs were given according to the truth table.
- iii) Observed the output of logic circuit and verify with truth table.

Result and discussion:

From the circuit, when the clock-pulse was sent to first flip-flop then Q_0 is 1 but Q_1, Q_2, Q_3 were 0. Again another pulse set, then it was in the next state, So on by this process, the circuit counted from 0 to 9. After 9 it returned the next state 0. The states are 0 to 9.

working precaution:

- i) Check the power supply.
- ii) Check the V_{cc} and ground of all IC's.
- iii) The wires were connected carefully.
- iv) The circuit was powered on before it was completed.
- v) The implementation was according to the circuit diagram.